

# **CSE 260M / ESE 260**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Michael Hall

# Reminder

- Studios can (and should) be done collaboratively!
- Homework should be done *independently*
  - Ok to discuss *ideas* and related work from *studio*
  - Should not discuss / share details of specific solutions

# This week & Misc.

- Hw #3B Posted / Due Sunday
- Calendar updates: Spring break dates were incorrect; Updated now!

# Last Lecture

- Sequential Circuits: Have a loop and outputs impact the inputs
- Bistable: Will hold one of two different states
  - May have some “metastable” condition
- SR-Latch: Cross-coupled NOR version
  - JLS version & time
  - Racing and unpredictable behavior


# SR Latch Issues: Hazardous Conditions!

- Short pulse
- R & S dropping at the same time

# Last Lecture

- D Latch: Transparent on high clock
- D Flip-Flop: Two D-latches that are transparent at opposite clock levels
  - Provide precise timing of data *acquisition* / storage
  - General focus: positive/rising edge triggers

# D-Flip-Flop Clock

 


[https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge\\_trigger.html](https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge_trigger.html)

# D Flip Flop is built from SR Latches

- Internal latch
  - Fails if pulses too short
  - Unstable if R/S drop at same time / too close
- Setup Time: Time needed before clock to ensure stable capture
- Hold Time: Time After clock edge value must be “held”



# Dff: Setup & Hold Time

 


# D Flip Flop Time Parameters

- $t_{setup}$ : Time D must be stable before clock
- $t_{hold}$ : Time D must be stable after clock
- $t_a$ : Aperture time ( $t_{setup} + t_{hold}$ ) —  
total window of time D needs to be stable around clock
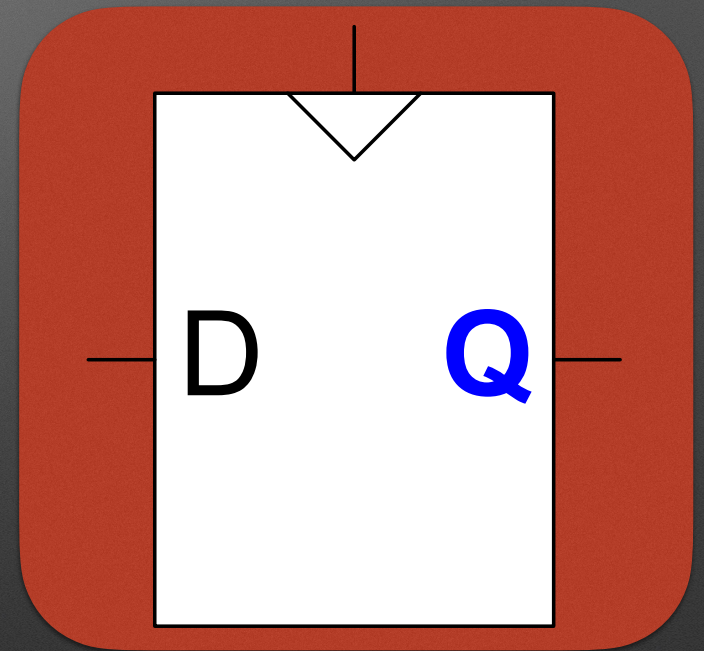
# Dff Time Parameters Relative to Clock

- $t_{pcq}$ : Propagation delay from Clock to Q (pcq)
- $t_{ccq}$ : Contamination delay from C to Q (ccq)



# Sequential & Synchronous Logic

- *Sequential* circuits
  - Can't be represented with a *simple* table of just inputs and outputs (Possibly a complex table of history of inputs and outputs)
  - Output depends on sequence of inputs and timing
- Synchronous Sequential Circuits
  - Sequential circuits with additional restrictions on form to improve predictability

# Synchronous Sequential Circuits

- Are *synchronized* by a common clock
- Uses registers (D Flip-Flops)
- Mix of registers and combinational logic
- All cycles include *at least one register*
- Goal: Impose predictable behavior!


# FSM Applications

- Things with modes or sequences of steps. Examples:
  - Washing Machine (fill, agitate, rinse, spin)
  - Stop lights & Traffic control: Green, Yellow, Red
  - Locks: Locked & unlocked
  - Computer programs: Playing game vs. on menu
  - Elevator controls (state = floor)
  - ...

# State Machine Diagram: Studio

Assume  
clock cycle of  
10s?

What does  
"clock" do?

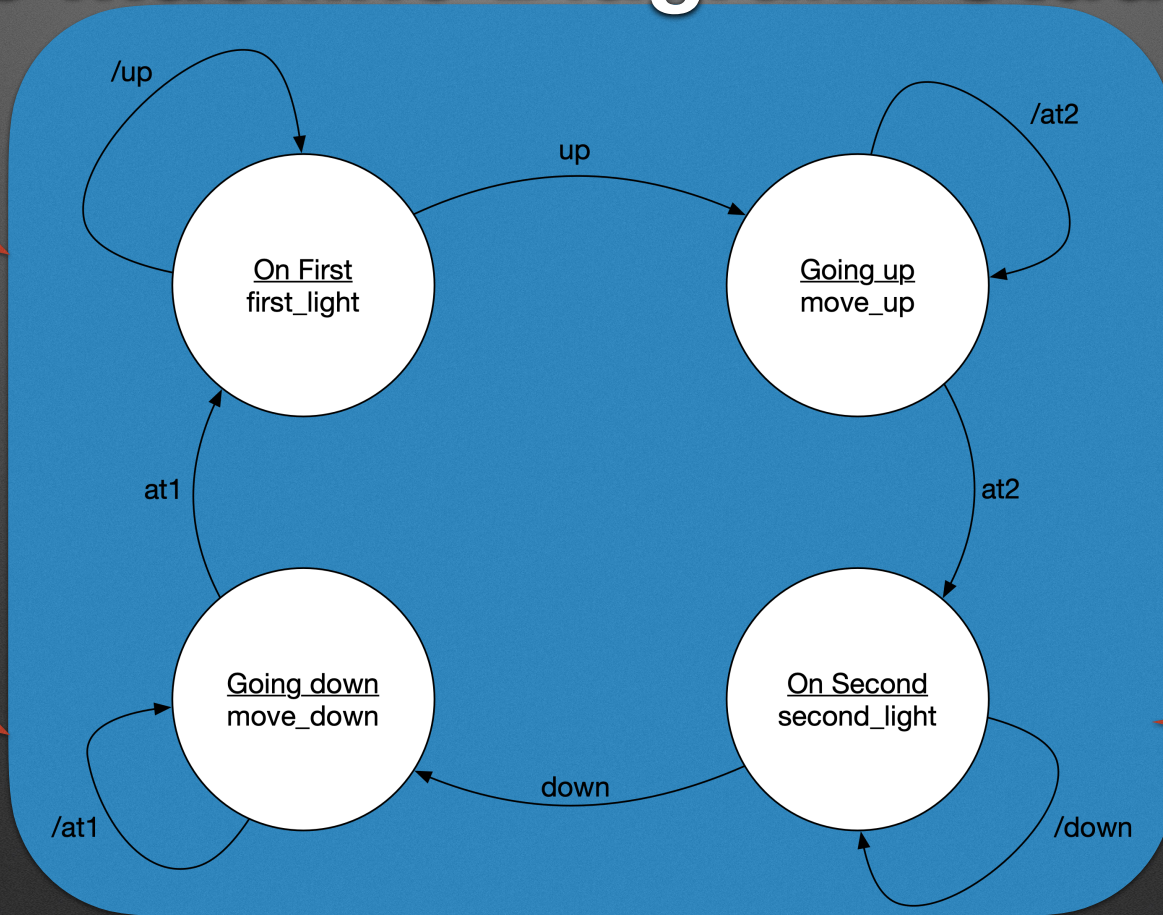

Vs 240s?


Can the  
clock be too  
short?

# Finite State Machines


- Can be realized with *synchronous* sequential circuits
  - Memory (registers/flip-flops) hold *encoded* state (represents the location or current bubble in diagram)
  - Combinational logic for:
    - Output control (the outputs in the bubbles)
    - Determine next state (the arrows)



# FSM: Mealy Machine

 

# FSM: Moore Machine Structure

 

# State Encodings

- “Art”
  - Encoding has impact on equations used
- Major flavors
  - Counting
  - One Hot

# Elevator: Examples

STATE NAME	BINARY COUNTING	ONE HOT
ON FIRST		
GOING UP		
ON SECOND		
GOING DOWN		

# Elevator: Examples Part 2

STATE NAME	BINARY COUNTING	ONE HOT
ON FIRST		
GOING UP		
ON SECOND		
GOING DOWN		

# Decoder

- Decoders...decode
  - $n$  bits of input to  $2^n$  distinct, mutually exclusive outputs
  - It's just ANDs/NOTs to select each distinct binary value


# Ex: 2-to-4 Decoder

# Working Elevator 1




# Elevator Rides Again: One Hot


# Review: Moore Machine Structure

 

# Review: Moore Machine Structure

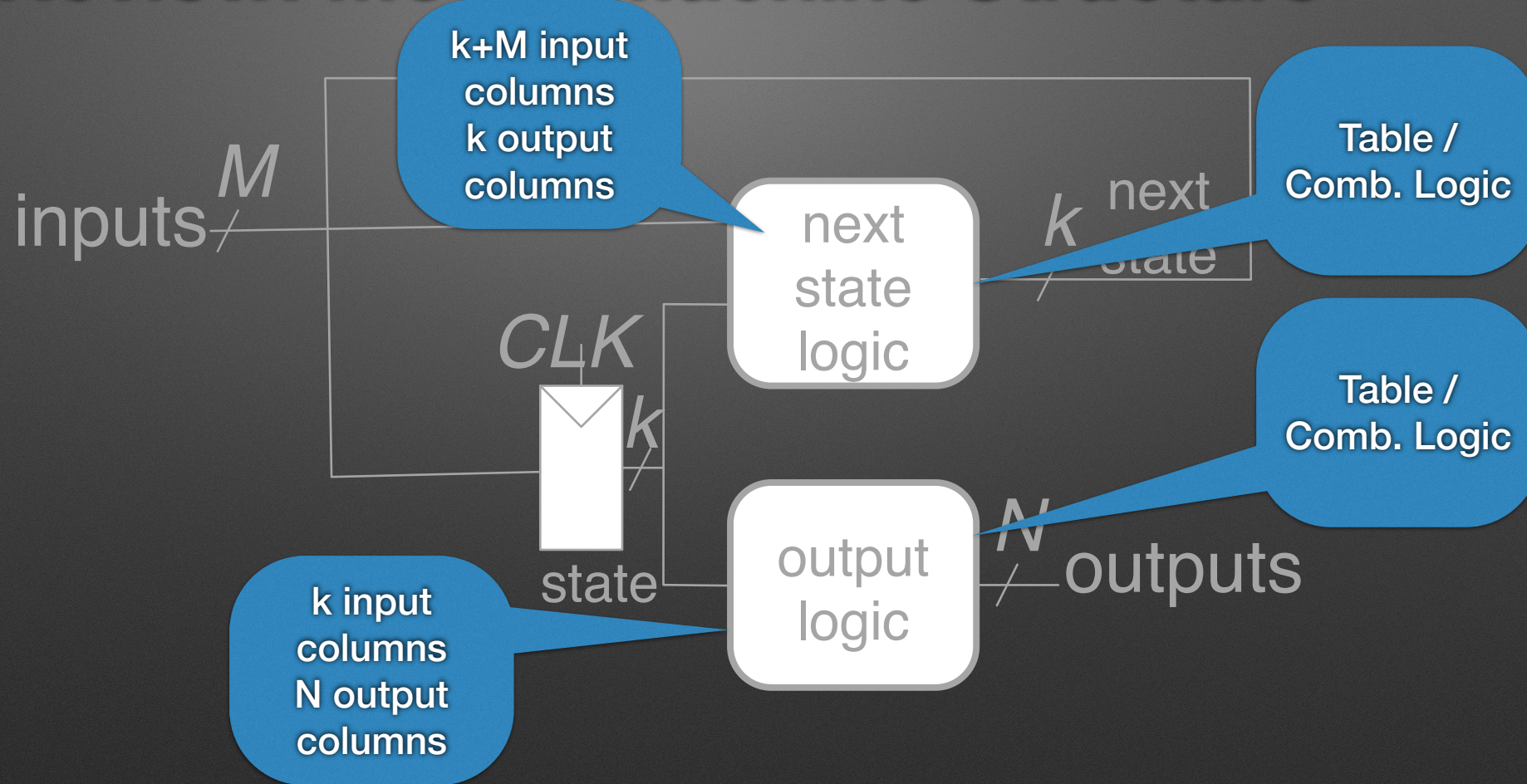



# Review: Dff Setup & Hold Time

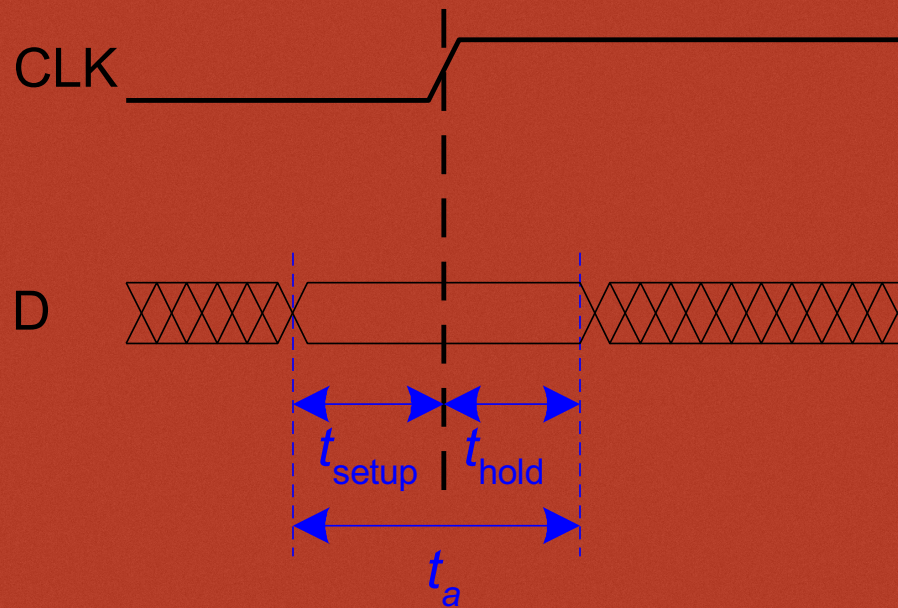
 
# Dff Time Parameters


- $t_{pcq}$ : Propagation delay from Clock to Q (pcq)
- $t_{ccq}$ : Contamination delay from C to Q (ccq)



 

 
# Setup Time Constraint

- Max time from R1 through CL
- R2's input needs to be stable  $t_{setup}$  before clock


 
# Setup Time Constraint


- Max time from R1 through CL
- R2's input needs to be stable  $t_{setup}$  before clock





 
# Hold Time Constraint

- Min time from R1 through CL
- R2's input must be stable  $t_{hold}$  after the clock


 
# Hold Time Constraint

- Min time from R1 through CL
- R2's input must be stable  $t_{hold}$  after the clock



# Synchronous Timing

- Must meet both
  - Setup Time Constraint
  - Hold Time Constraint

# Next Time

- Studio